

59

Vivekananda College of Engineering & Technology, Puttur
 [A Unit of Vivekananda Vidyavardhaka Sangha Puttur ®]
 Affiliated to VTU, Belagavi & Approved by AICTE New Delhi

CRM08

Rev 1.10

CS/AI

10/03/22

CONTINUOUS INTERNAL EVALUATION - 3

Dept: CS	Sem / Div: 3 CSA/B	Sub: Analog and Digital Electronics	S Code: 18CS33
Date: 17/03/2022	Time: 9:30-11:00 am	Max Marks: 50	Elective: N


Note: Answer any 2 full questions, choosing one full question from each part.

QN	Questions	Marks	RBT	CO's
PART A				
1 a	Derive the characteristics equations for T, SR and JK flip flops.	9	L3	CO3
b	Explain D flip-flop with timing diagram. Give the implementation of T flip flop from D flip flop.	8	L3	CO3
c	Explain the application of SR latch in switch debouncing technique.	8	L3	CO3
OR				
2 a	Construct SR latch using NAND gates and derive the characteristics equation for the same.	9	L3	CO3
b	Explain T flip flop with timing diagram. Realize T flip flop from JK flip flop.	8	L3	CO3
c	Explain master-slave JK flip flop operation with suitable diagrams.	8	L3	CO3
PART B				
3 a	Design Mod 5 counter using JK flip flop.	9	L3	CO4
b	With neat diagram, Explain the working of N-bit parallel adder with accumulator.	8	L3	CO4

c	With the help of state graph, state and transition tables and timing diagram, explain sequential parity checker.	8	L3	CO4
---	--	---	----	-----


OR

4 a	Design a random counter using T flip flop, whose transition graph is shown below	9	L3	CO4
-----	--	---	----	-----

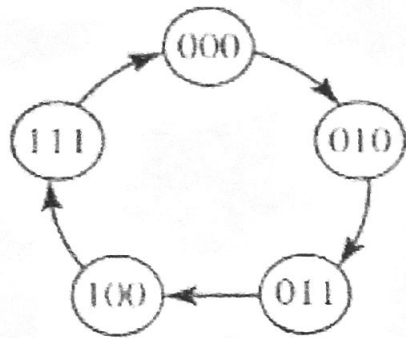

b	With neat diagram, explain 4 bit SISO shift register.	8	L3	CO4
---	---	---	----	-----

c	Differentiate between Moore and Mealy machines. Analyze the following Moore sequential circuit for an input sequence of $X=01101$ and draw the timing diagram.	8	L3	CO4
---	--	---	----	-----

 

Prepared by: Govindaraj P

Govindaraj P
10/03/22

[Signature]
11/02/22
HOD